

7447 BCD-SEVENSEGMNT

Madhu reddy

I. ABSTRACT

This paper shows how to use the 7447 BCD-Seven segment Display Decoder to learn Boolean logic using arduino uno.

II. COMPONENTS

The required components list is given in Table: I. and seven segment display is shown in Fig.2 and IC 7447 diagram is shown in Fig.1.

Components	Value	Quantity
IC	7447	1
seven segment display		1
Arduino	UNO	1
Jumper Wires		10
Breadboard		1

TABLE I



Fig. 1.

III. PROCEDURE

Truth Table for incrementing from 0 to 9 in seven segment display

Execute the arduino code without any errors.

After upload the code into hardware setup using arduino IDE platform with hex file.

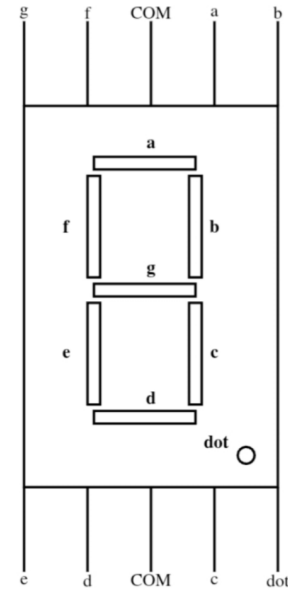


Fig. 2.

Z	Y	X	W	D	C	B	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

TABLE II

IV. RESULTS

- 1) Download the code given in the link below and execute them to see the output as shown in Fig.5.
- 2) <https://github.coM/madhureddy727/FWC-Assignments/tree/main/Assignment>

V. CONCLUSION

Hence implementation of 7447 IC, Seven segment display using arduino UNO is done.

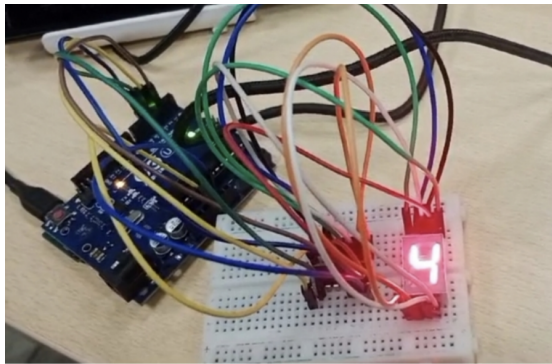


Fig. 3.