

Assembly Assignment

Madhu Reddy

I. ABSTRACT

This paper explains about the question asks for the 16-bit two's complement binary representation of the decimal number -28. The correct binary sequence must be identified. In two's complement, negative numbers are represented by inverting all bits of the absolute value of the number and adding 1 to the least significant bit. The question can be implemented using assembly code in arduino uno and the correct binary sequence must be displayed in LCD [Liquid Crystal Display] - JHD 162A.

II. COMPONENTS

The required components list is given in Table: I., pin diagram of LCD JHD 162A is shown in Fig.1.

Components	Value	Quantity
sevensseg	JHD 162A	1
Arduino	UNO	1
Jumper Wires		20
Breadboard		1

TABLE I

III. PROCEDURE

- 1) Pin Configuration of sevensseg.
- 2) Make connections of arduino uno to sevensseg
- 3) Execute the arduino code in nvim editor using avra filename.tex command.
- 4) After upload the code into hardware setup using arduino IDE platform.

IV. RESULTS

- 1) Download the codes given in the link below and execute them to see the output as shown in figure 3.
- 2) <https://github.com/madhureddy727/FWC-Assignments>

V. CONCLUSION

Hence implementation of assembly code in arduino uno and the correct binary sequence is displayed on LED[seven segment] is done .

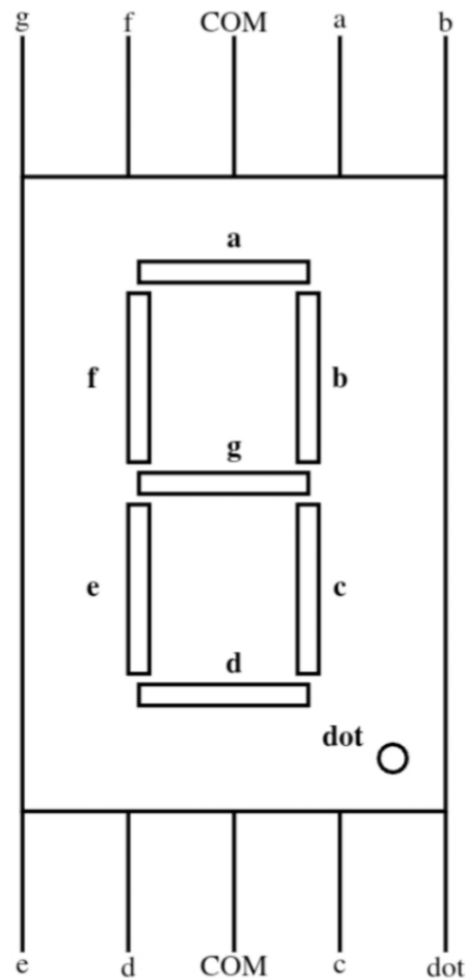


Fig. 1.

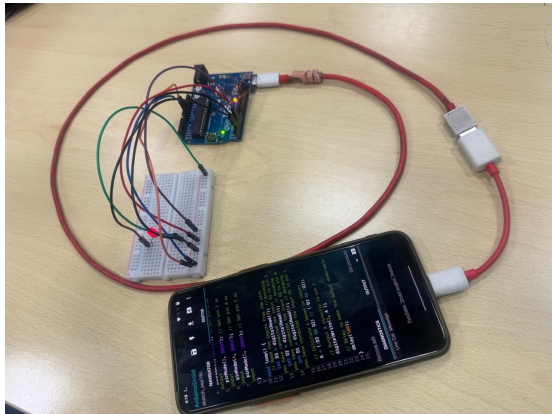


Fig. 2.